
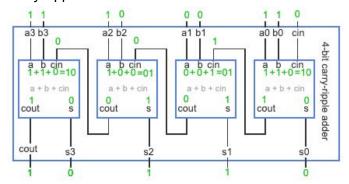
## 4.1 Adders

- Binary adders, 1+1 carries 1
- Computes A+B
  - A, B are N-bit numbers
  - Carry-ripple adder



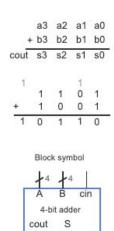

- \_
- N-bit carry-ripple adder adds two N-bit numbers
- N is the size of each input
- C<sub>out</sub> is the carry bit, 1 indicates a carry

- Full adder
  - circuit that adds three bits and generates a sum and carry-out.
  - Half adder
    - circuit that adds two bits and generates a sum and carry-out bit
  - An N-bit carry-ripple adder is constructed with N full adders
- Incrementer
  - Adds 1 to a number (Adds 1 to input A)
  - Usually use half adder to implement incrementer but Full adder also works, but it requires larger circuits

## 4.2 Signed numbers in Binary

- Unsigned positive only
- Signed both positive and negative
- Use the left bit for the sign, 0 positive, 1 negative
- Two's complement signed number representation
  - For negative numbers, calculate its complement
    - Invert 1 and 0
    - Add 1 to the result
  - Add two numbers up, and ignore the carry bit
  - example


Complement: invert bits, add 1.

## Replace with complement:

- More examples
  - 1011, negative because the left bit is 1
  - 1001, negative because the left bit is 1, in decimal
    - 0110 + 1 = 0111
    - Magnitude is 7, yields to -7 in decimal
  - -3 in eight-bit two's complement representation is
    - 00000011
    - 111111100 + 1
    - 11111101
- Allows adder to deal with negative number additions
  - 3 + -4
  - 0011 + 1100
  - 1111 (two's complement representation)
  - 0000 + 1 = 0001, magnitude is 1, in decimal is -1
- Overflow
  - Adding two positives, or adding two negatives, may yield a value that can't be represented in the given number of bits
  - Example
    - 0001 + 1111 = 0000
    - Adding a negative number and a positive number cannot result in overflow
    - 0111 + 0110 = 1101 (-3)
    - 6 + 7 results overflow
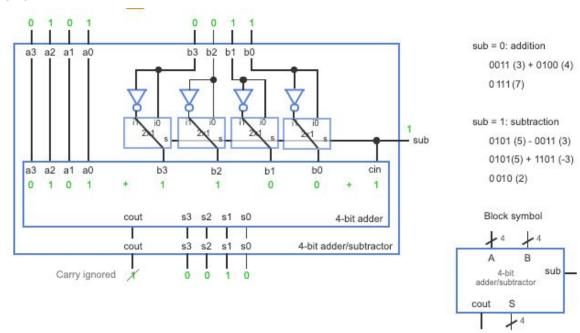
## **4.3 Subtractors**

- Computes A B
- Using two's complement representation for (-B)
- Because two's-complement representation performs subtraction by complementing and adding, a single adder circuit can perform either addition or subtraction, thus saving circuit size



-