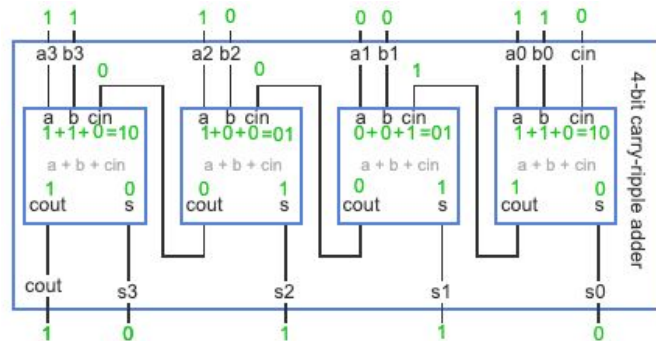


## 4.1 Adders

- Binary adders, 1+1 carries 1
- Computes A+B
  - A, B are N-bit numbers
  - Carry-ripple adder




	a3	a2	a1	a0
	+ b3	b2	b1	b0
cout	s3	s2	s1	s0

	1			1
	1	1	0	1
+	1	0	0	1
	1	0	1	0

Block symbol

 

- N-bit carry-ripple adder adds two N-bit numbers
- N is the size of each input
- $C_{out}$  is the carry bit, 1 indicates a carry

A = 1111, B = 0001

☐ cout = 0  
s3s2s1s0 = 0000

☐ cout = 1  
s3s2s1s0 = 1111

☒ cout = 1  
s3s2s1s0 = 0000

### - Full adder

- circuit that adds three bits and generates a sum and carry-out.
- Half adder
  - circuit that adds two bits and generates a sum and carry-out bit
- An N-bit carry-ripple adder is constructed with N full adders

### - Incrementer

- Adds 1 to a number (Adds 1 to input A)
- Usually use half adder to implement incrementer but Full adder also works, but it requires larger circuits

## 4.2 Signed numbers in Binary

- Unsigned - positive only
- Signed - both positive and negative
- Use the left bit for the sign, 0 - positive, 1 - negative
- **Two's complement signed number representation**
  - For negative numbers, calculate its complement
    - Invert 1 and 0
    - Add 1 to the result
  - Add two numbers up, and ignore the carry bit
  - example

Complement: invert bits, add 1.

$$\begin{array}{r} 0011 \text{ (3) has complement: } (0011)' + 1 \\ 1100 + 1 \\ \hline 1101 \end{array}$$


Replace with complement:

$$\begin{array}{r} 0101 \text{ (5)} \\ - 0011 \text{ (3)} \\ \hline 0010 \text{ (2)} \end{array} \quad \begin{array}{r} 0101 \text{ (5)} \\ + 1101 \text{ (-3)} \\ \hline \cancel{1}0010 \text{ (2)} \text{ ignore carry} \end{array}$$

- 
- More examples
  - 1011, negative because the left bit is 1
  - 1001, negative because the left bit is 1, in decimal
    - $0110 + 1 = 0111$
    - Magnitude is 7, yields to -7 in decimal
  - -3 in eight-bit two's complement representation is
    - 00000011
    - $11111100 + 1$
    - 11111101
- Allows adder to deal with negative number additions
  - $3 + -4$
  - $0011 + 1100$
  - 1111 (two's complement representation)
  - $0000 + 1 = 0001$ , magnitude is 1, in decimal is -1
- **Overflow**
  - Adding two positives, or adding two negatives, may yield a value that can't be represented in the given number of bits
  - Example
    - $0001 + 1111 = 0000$
    - Adding a negative number and a positive number cannot result in overflow
    - $0111 + 0110 = 1101$  (-3)
    - $6 + 7$  results overflow

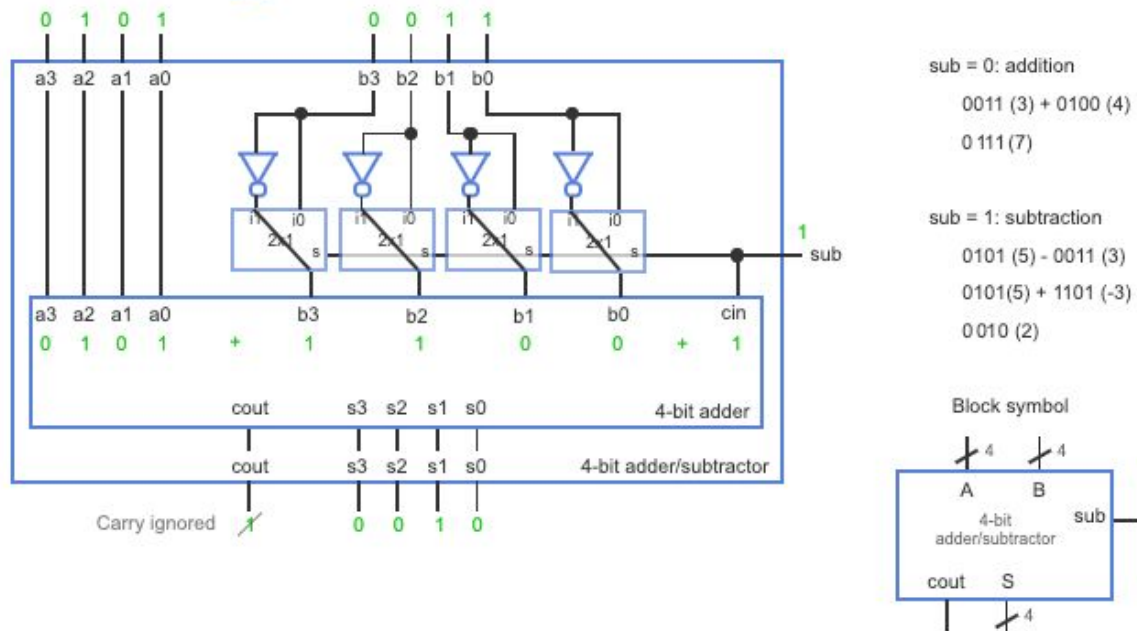
### 4.3 Subtractors

- Computes  $A - B$
- Using two's complement representation for  $(-B)$
- Because two's-complement representation performs subtraction by complementing and adding, a single adder circuit can perform either addition or subtraction, thus saving circuit size


 
### 4.4 Comparators


- Def: compares two numbers, indicating whether the numbers are equal, or which number is greater.



- Compare bit by bit
- Carry-ripple comparator
  - compares two N-bit numbers from left to right, with the result of each digit's comparison "rippling" to the next digit

- For each digit, a **one-bit comparator** compares two bits a and b only if the eq input was 1 from the higher digit
- else just passing along a gt 1 or an lt 1

#### 4.5 N-bit Muxes

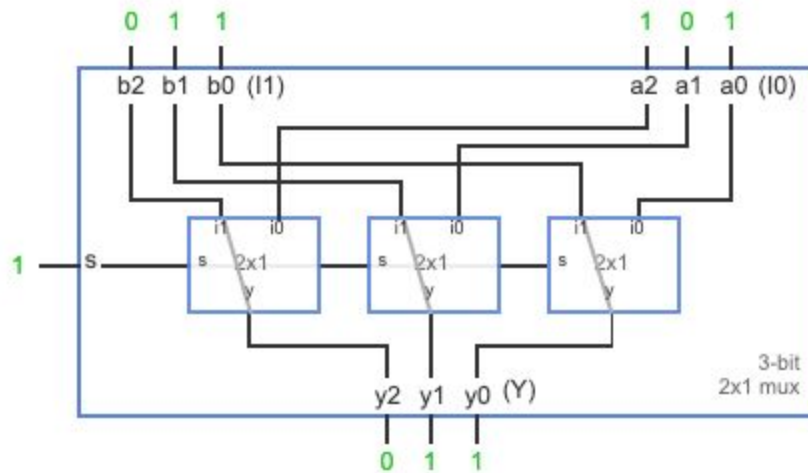


- 3-bit 2x1 Mux.
 
#### 4.6 Load Registers

- Load register design
- Only want to load a register on certain clock cycles, rather than every clock cycle
- Registers come along with a control input "ld" or "load"
- Implementing such a load register can be done using 2x1 muxes

For the given values of D, Id, and clk, indicate the register's Q value.



1) (a)

Q =

**Check**

[Show answer](#)

**Correct**

When Id is 1 and the clock rises, D is loaded into the register.

2) (b)

Q =

**Check**

[Show answer](#)

**Correct**

When Id is 1, the new value of D is loaded into the register on the rising clock edge.

3) (c)

Q =

**Check**

[Show answer](#)

**Correct**

When Id is 0 and the clock rises, the present value is maintained.

4) (d)

Q =

**Check**

[Show answer](#)

**Correct**

When Id is 1, the new value of D is loaded into the register on the rising clock edge.

-

- An N-bit **load register** (such as an 8-bit load register or just 8-bit register) stores N bit values
- Loading new bit values when a clock input rises **if a load input is 1**
- A load input (Id) indicates when the register should be loaded.
- A reset input (rst) may exist that indicates that the register's bits should be reset to 0 (having priority over Id)